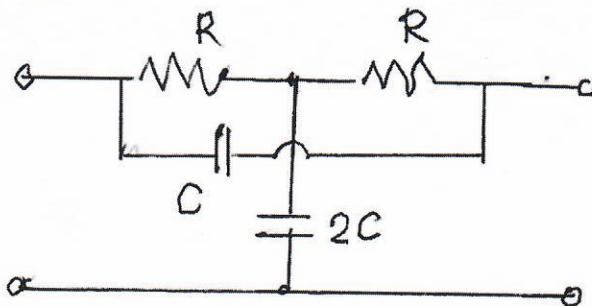


MIDTERM EXAMINATION

October 19, 2022


Open Book

1. Find the short-circuit parameters of the circuit shown below. Assume $R = 5 \text{ k}\Omega$, $C = 10 \text{ pF}$ and $f = 3 \text{ MHz}$.





P.43
5
P.45

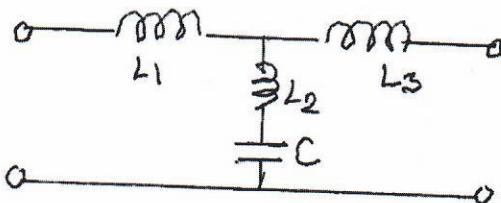2. Two of the short-circuit admittances of the circuit shown are $y_{11} = y_{22} = (7s^2 + 1)/(16s^3 + 4s)$. Find all element values.




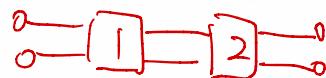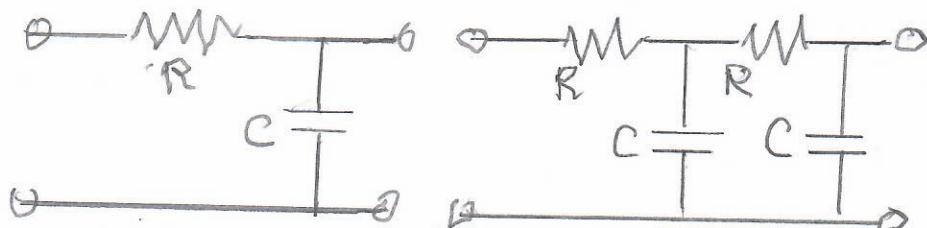3. Find the chain matrices of the two-ports shown below.



3. Find the chain matrices of the two-ports shown below.


3.

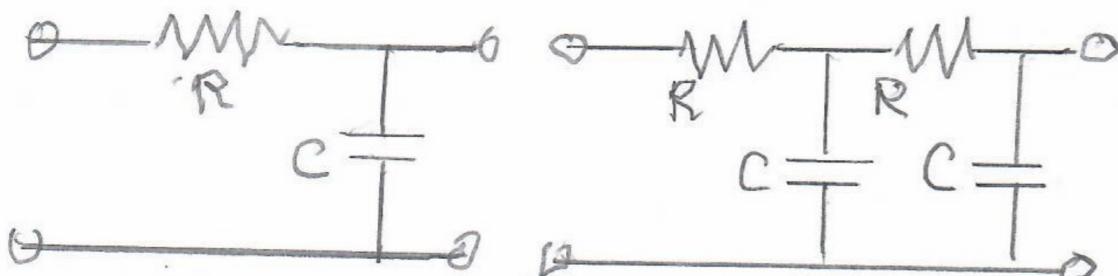


$$T = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} SCR+1 & R \\ SC & 1 \end{bmatrix}$$

P.43

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = SCR+1$$

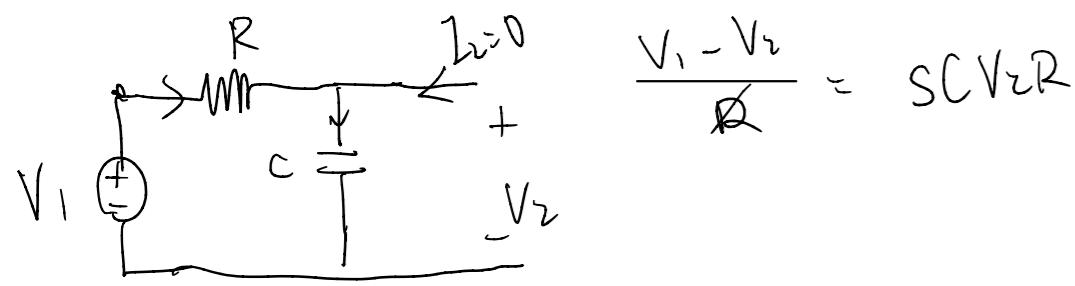


$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = SC$$

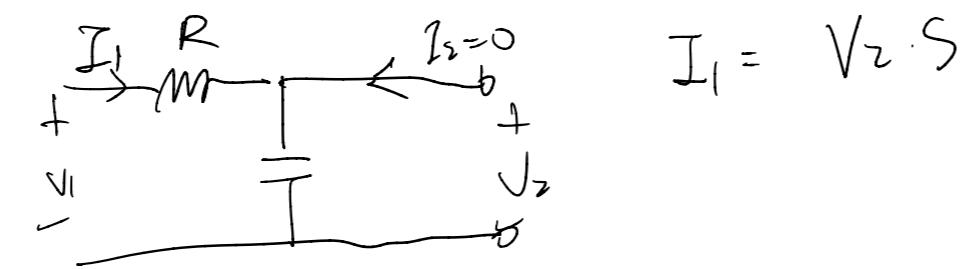


$$I_1 = V_2 \cdot SC$$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} = R$$

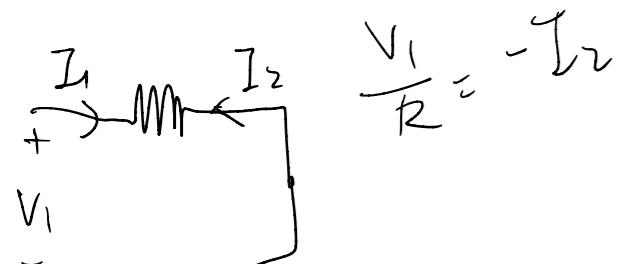

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0} = 1$$

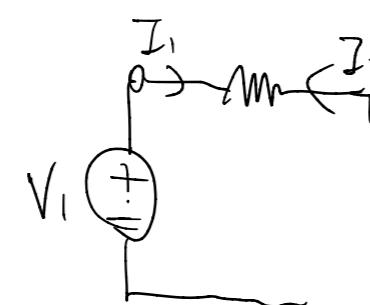

Since it's cascade connection
and two R has same value, two C same value
chain matrices will be T^2


$$T^2 = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A^2 + BC & AB + BD \\ AC + DC & BC + D^2 \end{bmatrix}$$

$$= \begin{bmatrix} (SCR+1)^2 + RSC & (SCR+1)R + R \\ (SCR+1)SC + SC & SCR + 1 \end{bmatrix}$$

$S^2 C^2 R + 2SC$


$$SCR^2 + 2R$$

1

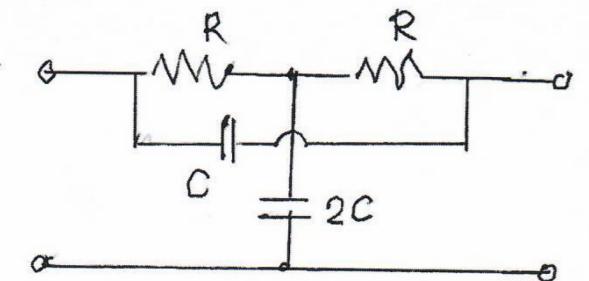


$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \rightarrow \begin{aligned} I_1 &= y_{11} \cdot V_1 + y_{12} V_2 \\ I_2 &= y_{21} \cdot V_1 + y_{22} V_2 \end{aligned}$$

First Part

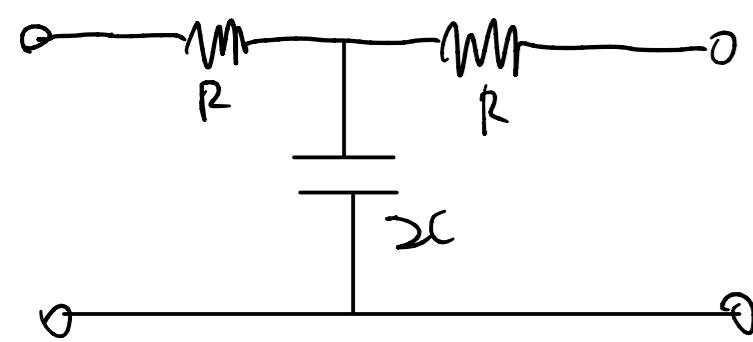


$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = \frac{1}{2SR^2C + 2R}$$
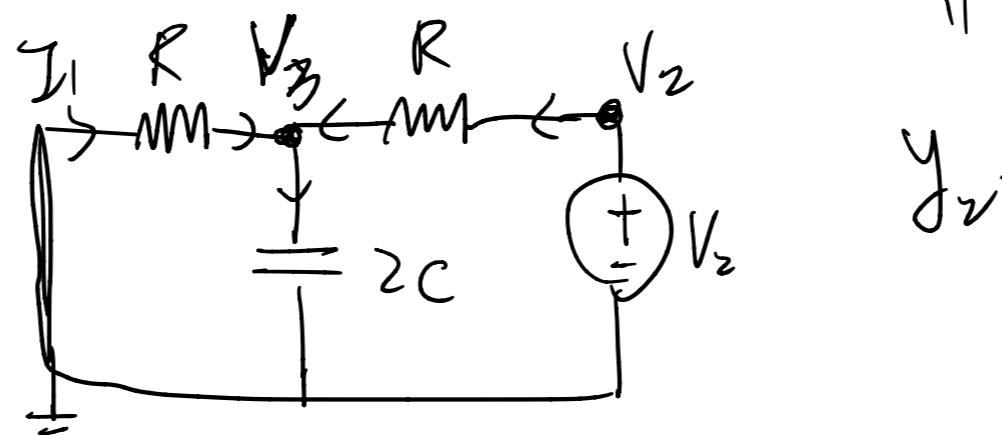
$$Y_A = \begin{bmatrix} y_{11A} & y_{12A} \\ y_{21A} & y_{22A} \end{bmatrix}$$



$$y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{2SRC+1}{2SR^2C+2R} = y_{22}$$
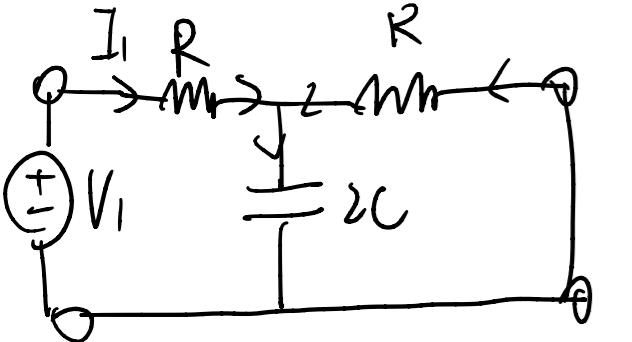
$$I_1 = \frac{V_1}{R + (R \parallel \frac{1}{2SC})}$$



$$I_1 = \frac{V_1}{\frac{2SR^2C+2R}{2SRC+1}}$$

$$\left\{ \begin{aligned} V_3 &= -I_1 R \end{aligned} \right.$$

$$\left\{ \begin{aligned} I_1 + \frac{V_2 - V_3}{R} &= V_3 SCZ \end{aligned} \right.$$


$$\left\{ \begin{aligned} V_2 &= -I_1 R + \frac{-I_1 R}{(R \parallel \frac{1}{SC})} \end{aligned} \right.$$

$$= \begin{bmatrix} \frac{2SRC+1}{2SR^2C+2R} & \frac{1}{2SR^2C+2R} \\ \frac{1}{2SR^2C+2R} & \frac{2SRC+1}{2SR^2C+R} \end{bmatrix}$$

$$R + \left(R // \frac{1}{2SC} \right) = \frac{\frac{R}{2SC}}{R + \frac{1}{2SC}} = \frac{R}{2SC \cdot \left(\frac{2S+1}{SC} \right)}$$

$$= \frac{R}{2SRC + 1} = \frac{2SRC^2 + 2R}{2SRC + 1}$$

Second Part

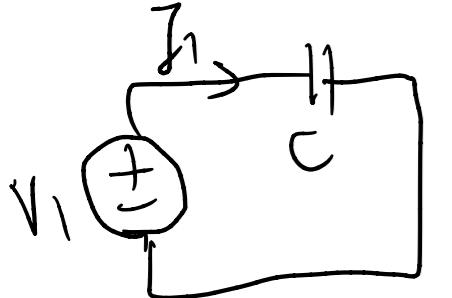

$$y_{11b} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = SC = y_{12b} = -y_{21b} = -y_{22b}$$

$$\begin{aligned} I_1 + \frac{V_2}{R} + \frac{I_1 R}{R} &= -I_1 R S C \cdot 2 \\ 2I_1 + 2SRC I_1 + V_2/R &= 0 \\ 2(SC + 1)R I_1 + \frac{V_2}{R} &= 0 \end{aligned}$$

$$\frac{I_1}{V_2} = \frac{1}{2SRC^2 + 2R}$$

$$y_b = \begin{bmatrix} SC & -SC \\ -SC & SC \end{bmatrix}$$


P.46

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} + \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} y_{11a} & y_{12a} \\ y_{21a} & y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} + \begin{bmatrix} y_{11b} & y_{12b} \\ y_{21b} & y_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} = \begin{bmatrix} y_{11a} + y_{11b} & y_{12a} + y_{12b} \\ y_{21a} + y_{21b} & y_{22a} + y_{22b} \end{bmatrix} \begin{bmatrix} V_1 \\ V_z \end{bmatrix}$$

$$R = 5k\Omega, C = 10 \text{ pF}, f = 3 \text{ MHz}, SC = j\omega C = 2\pi f C = 2\pi \times 3 \times 10^6 \times 10 \times 10^{-12} = 6\pi \times 10^{-5}$$

$$\left\{ \begin{array}{l} \frac{2SRC+1}{2SR^2C+R} + SC \\ \frac{1}{2SR^2C+2R} - SC \\ \frac{1}{2SR^2C+2R} - SC \end{array} \right. \quad \left. \begin{array}{l} \frac{2 \times 6\pi \times 10^{-5} \times 5 \times 10^3 + 1}{2 \cdot 6\pi \times 10^5 \times 25 \times 10^6 + 5 \times 10^3} + 6\pi \times 10^{-5} \\ \frac{2 \times 6\pi \times 10^{-5} \times 5 \times 10^3 + 1}{2 \cdot 6\pi \times 10^5 \times 25 \times 10^6 + 5 \times 10^3} + 6\pi \times 10^{-5} \end{array} \right\}$$

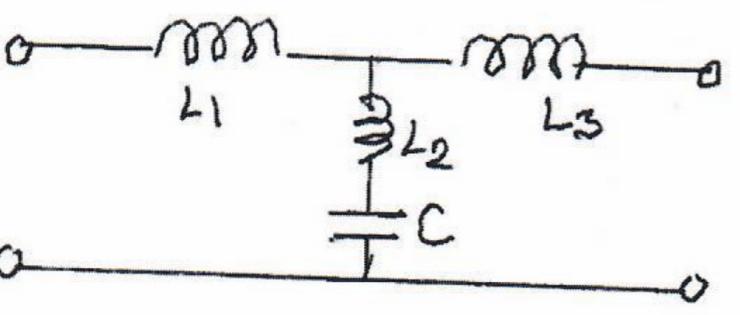2. Two of the short-circuit admittances of the circuit shown are $y_{11} = y_{22} = (7s^2 + 1)/(16s^3 + 4s)$. Find all element values.



$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$y_{11} = y_{22} = \frac{9s^2 + 1}{s(16s^3 + 4)}$$

$$sL_2 + \frac{1}{sC} = \frac{s^2CL_2 + 1}{sC}$$

$$y_{11} = y_{22} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

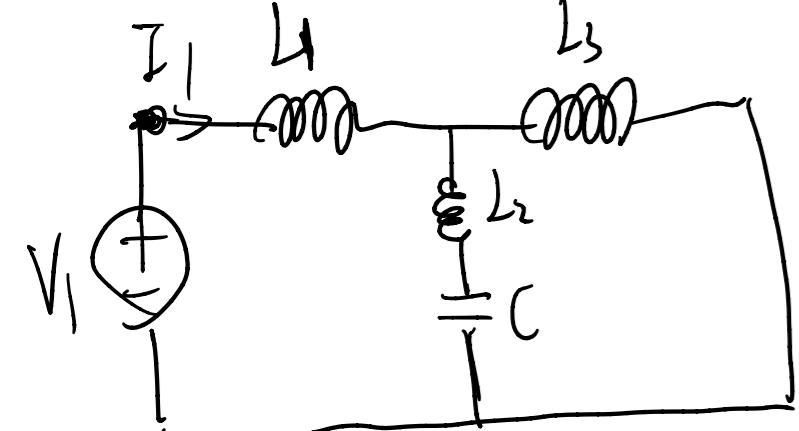

$$I_1 = \frac{V_1}{sL_1 + \left[\left(sL_2 + \frac{1}{sC} \right) // sL_3 \right]}$$

$$\left(sL_2 + \frac{1}{sC} \right) // sL_3 = \frac{s^3CL_2L_3 + sL_3}{s^2C(L_2 + L_3) + 1}$$

$$\left[\left(sL_2 + \frac{1}{sC} \right) // sL_3 \right] + sL_1 =$$

$$\frac{s^3CL_2L_3 + sL_3 + s^3C(L_2 + L_3)L_1 + sL_1}{s^2C(L_2 + L_3) + 1} = \frac{s \left[s^2C(L_1L_2 + L_1L_3 + L_2L_3) + (L_1 + L_3) \right]}{s^2C(L_2 + L_3) + 1}$$

$$= \frac{s(16s^2 + 4)}{9s^2 + 1}$$

$$\left\{ \begin{array}{l} C(L_2 + L_3) = 7 \\ L_1 + L_3 = 4 \\ L_1 L_2 + L_1 L_3 + L_2 L_3 = 16 \\ L_1 = L_3 \end{array} \right.$$



$$\left\{ \begin{array}{l} L_1 = L_3 = 2 \text{ H} \\ C(L_2 + 2) = 7 \rightarrow C = \frac{7}{5} = 1.4 \text{ F} \\ 4L_2 = 12 \rightarrow L_2 = 3 \text{ H} \end{array} \right. \quad \#$$