

Mock Final Examination


ECE 580

December 1, 2021


1. Find the transfer function for the bilinear filter stage shown below:

(a) For ideal opamp;

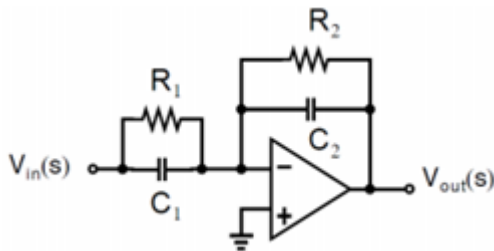
(b) For a finite-gain and bandwidth opamp with the gain function $A(s) = A_o / (1 + sA_o/w_u)$.



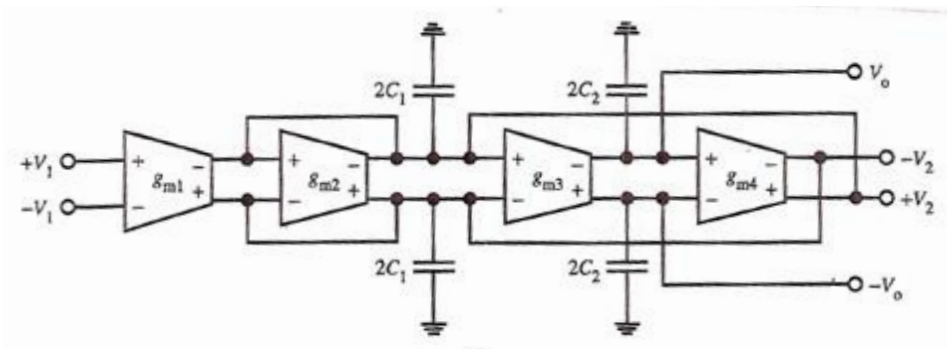2. Find the voltage gains V_o/V_1 and V_2/V_1 of the Gm-C biquad shown.



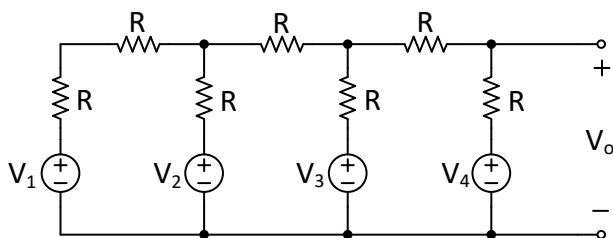3. In the circuit shown, $V_1 = V_2 = 1V$ and $V_3 = V_4 = 2V$. How much is V_o ?




Hints: Use inter-reciprocity; Analyze \hat{N} from output to input.


1. Find the transfer function for the bilinear filter stage shown below:

(a) For ideal opamp;

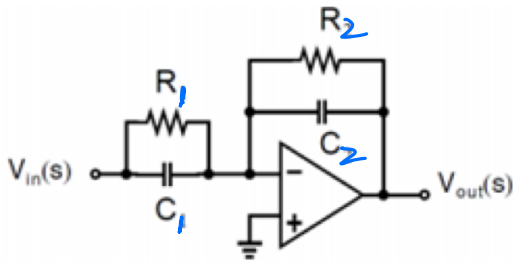(b) For a finite-gain and bandwidth opamp with the gain function $A(s) = A_0 / (1 + sA_0/w_0)$.


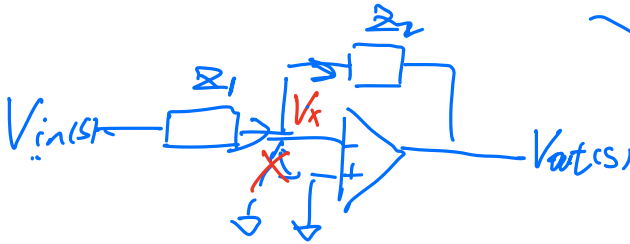
$$Z_1 = R \parallel \frac{1}{sC} = \frac{R \cdot \frac{1}{sC}}{R + \frac{1}{sC}} = \frac{R}{sRC + 1}$$



$$\frac{V_{out}(s)}{V_{in}(s)} = - \frac{R_2}{R_1} \frac{1 + R_1 C_1 s}{1 + R_2 C_2 s}$$


$$\begin{cases} \frac{V_{in} - V_x}{Z_1} = \frac{V_x - V_{out}}{Z_2} \\ V_{out} = -A(s) V_x \end{cases}$$

$$A(s) = \frac{A_0}{1 + sA_0/w_0}$$

$$\Rightarrow \frac{V_{out}(s)}{V_{in}(s)} = - \frac{R_2}{R_1} \frac{A_0}{1 + A_0} \frac{1 + R_1 C_1 s}{1 + R_2 C_2 s} \frac{1}{1 + s/w_0}$$

2. Find the voltage gains V_o/V_1 and V_2/V_1 of the Gm-C biquad shown.

Gm-C

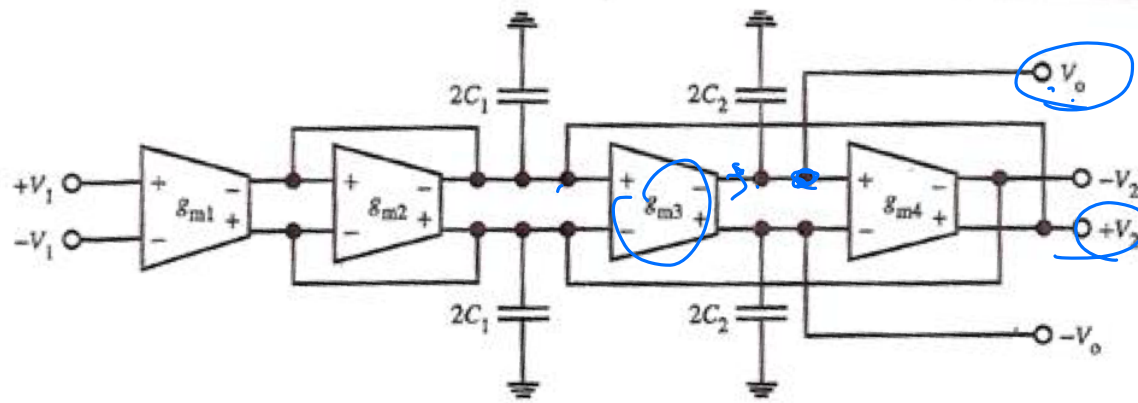

Gm-C

↓

VCCS

V C

$$\frac{V_o}{V} : \begin{cases} (-V_1 g_{m1} - V_2 g_{m2} + V_o g_{m4}) \cdot \frac{1}{sC_1} = V_2 \\ (-g_{m3} V_2) \cdot \frac{1}{sC_2} = V_o \end{cases}$$

$$\frac{V_o}{V} / \frac{V_2}{V_1}$$