

**MIDTERM EXAMINATION**


**ECE 580**


October 16, 2024

Open Book

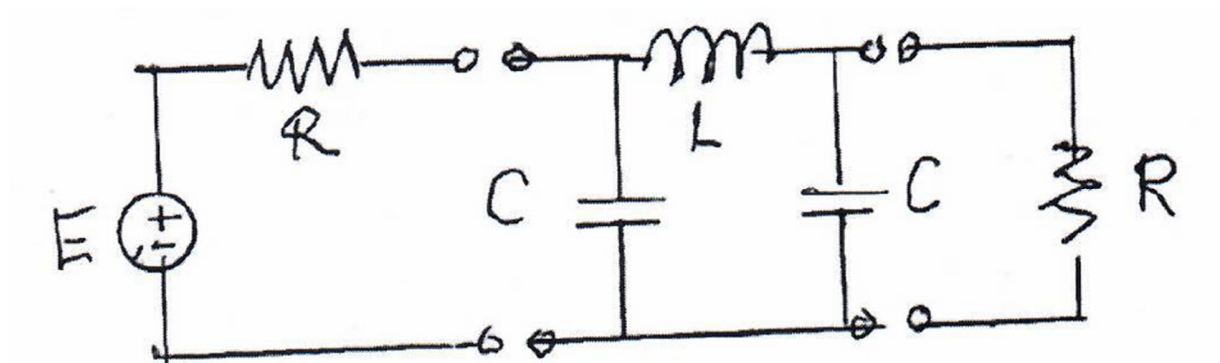1. a. Find the impedance parameters of the LC two-port shown.
- b. Find the voltage gain  $A_v(s)$  and the transducer factor  $H(s)$  for the doubly terminated two-port.
- c. Find the reflection coefficient  $\rho_1(s)$  and  $\rho_2(s)$ .

*For extra credit:* find the values of  $H(j\omega)$  and  $\rho_1(j\omega)$  for  $R = 50 \Omega$ ,  $\omega = 100 \text{ Mrad/s}$ ,  $L = 10 \text{ nH}$  and  $C = 1 \text{ pF}$ .



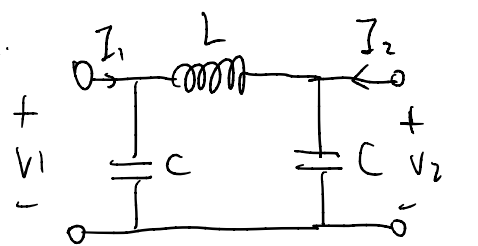a.  From midterm 2023, we got the chain matrix is

$$T = \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} s^2LC+1 & sL \\ sC(s^2LC+2) & s^2LC+1 \end{bmatrix}$$

we can convert  $T$  to  $Z$

$$\rightarrow \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{A}{C} & \frac{AD-BC}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix} = \begin{bmatrix} \frac{s^2LC+1}{sC(s^2LC+2)} & \frac{(s^2LC+1)^2 - s^2LC(s^2LC+2)}{sC(s^2LC+2)} \\ \frac{1}{sC(s^2LC+2)} & \frac{s^2LC+1}{sC(s^2LC+2)} \end{bmatrix}$$

$$= \begin{bmatrix} \frac{s^2LC+1}{sC(s^2LC+2)} & \frac{1}{sC(s^2LC+2)} \\ \frac{1}{sC(s^2LC+2)} & \frac{s^2LC+1}{sC(s^2LC+2)} \end{bmatrix} \#$$

b.  $A_v(s) = \frac{V_2(s)}{E(s)} = \frac{R_L}{AR_L + B + CR_LR_L + DR_G}$

$$= \frac{R}{(s^2LC+1)R + sL + sC(s^2LC+2)R^2 + s^2CLR + R}$$

$$= \frac{1}{s^3RLC^2 + 2s^2LC + s(\frac{L}{R} + 2RC) + 2} \#$$

$$H(s) = \frac{\sqrt{R_L/R_C}}{2A_v} = \frac{\sqrt{R/R}}{2A_v}$$

$$= s^3 RLC^2 + 2s^2 LC + s\left(\frac{L}{R} + 2RC\right) + 2 \quad \#$$

Extra Credits:  $R = 50 \Omega$ ,  $\omega = 10^8 \text{ rad/s}$ ,  $L = 10^{-8} \text{ H}$ ,  $C = 10^{-12} \text{ F}$

$$H(s) = (10^8 j)^3 \cdot 50 \times 10^{-8} \times 10^{-12} + 2 \cdot (10^8 j)^2 \cdot 10^{-8} \times 10^{-12} \\ + (j \times 10^8) \left( 10^{-8} \cdot \frac{1}{50} + 2 \cdot 50 \times 10^{-12} \right) + 2$$

$$\approx 2 + 0.03j \quad \#$$

$$C. \quad \rho(s) = \frac{Z_{in}(s) - Z_0}{Z_{in}(s) + Z_0}, \quad Z = \begin{bmatrix} \frac{s^2 LC + 1}{sC(s^2 LC + 2)} & \frac{1}{sC(s^2 LC + 2)} \\ \frac{1}{sC(s^2 LC + 2)} & \frac{s^2 LC + 1}{sC(s^2 LC + 2)} \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$$

$$\rho_1(s) = \frac{Z_{in} - Z_{source}}{Z_{in} + Z_{source}} = \frac{Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22}}}{Z_{11} + \frac{Z_{12} Z_{21}}{Z_{22}}} \quad \#$$

$$Z_{in}(s) = Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22} + Z_L}$$

$$\rho_2(s) = \frac{Z_{out}(s) - Z_L}{Z_{out}(s) + Z_L} = \frac{Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11}}}{Z_{22} + \frac{Z_{12} Z_{21}}{Z_{11}}} \quad \#$$

$$Z_{out}(s) = Z_{22} - \frac{Z_{12} Z_{21}}{Z_{11} + Z_s}$$