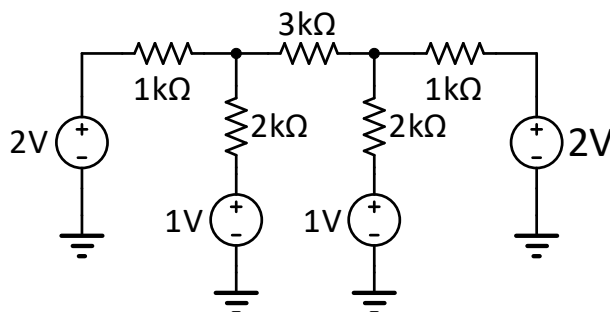


# FINAL EXAMINATION


## ECE 580

December 14, 2023

1. Analyze the circuit shown. **Warning:** look for a shortcut!!



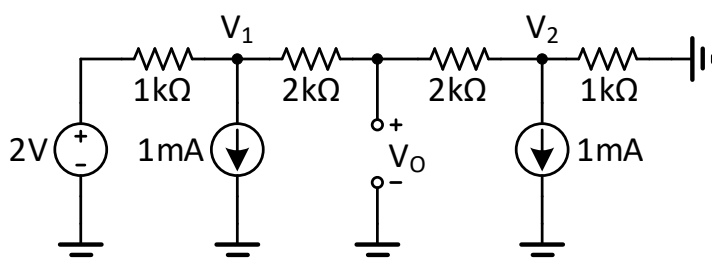2. Analyze the circuit shown using inter-reciprocity.




For extra credit, find  $V_1$  and  $V_2$ .

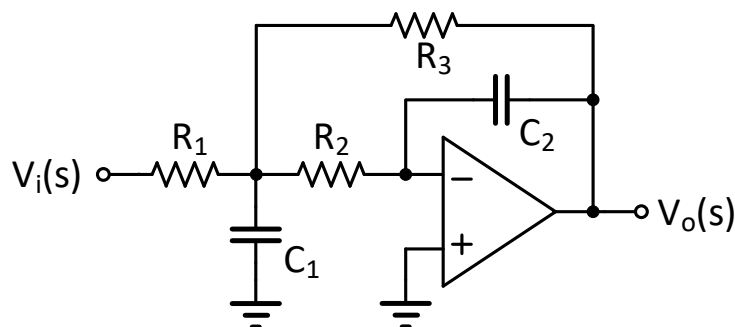3. The Rauch filter shown has a transfer function (assume ideal opamp)



$$H(s) = \frac{1}{s^2 \cdot R_1 \cdot R_2 \cdot C_1 \cdot C_2 + s \cdot C_2 \cdot \left( R_1 + R_2 + \frac{R_1 \cdot R_2}{R_3} \right) + \frac{R_1}{R_3}}$$

If  $R_1 = 2R_2 = 2R_3$  and pole  $Q$  is  $Q = 1/\sqrt{3}$ , what should be the ratio  $C_1/C_2$ ?



For extra credit, find the requirements for the DC gain  $A_0$  and the pole  $Q$  so that the minimum capacitance spread ( $C_1/C_2$  or  $C_2/C_1$ ) can be 1. **Hint:** consider the requirements for  $A_0$  and  $Q$  so that there is real solution for  $R_2/R_3$  when  $C_1 = C_2$ .

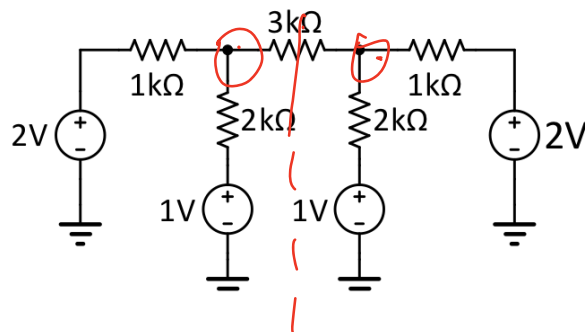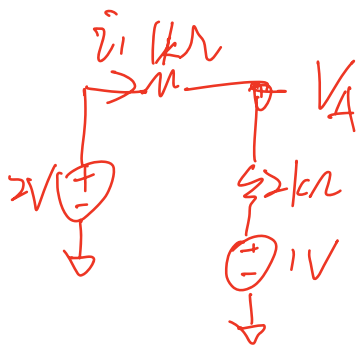1. Analyze the circuit shown. **Warning:** look for a shortcut!!



$$\frac{2-1}{3} = \frac{1}{3} \text{ mA}$$

$$V_A = 1 + \frac{1}{3} \times 2$$

$$= \frac{5}{3} \text{ V}$$

$$\frac{2-V_A}{1} = i_1$$

$$\frac{1-V_A}{2} = i_2$$

$$\frac{V_A-V_B}{3} = i_3$$

$$i_1 + i_2 = i_3$$

$$\frac{2-V_B}{1} = i_6$$

$$\frac{1-V_B}{2} = i_5$$


$$\frac{V_B-V_A}{3} = -i_4$$

$$i_4 + i_5 + i_6 = 0$$

$$V_A = V_B$$

$$V_A = \frac{5}{3} \text{ V}$$

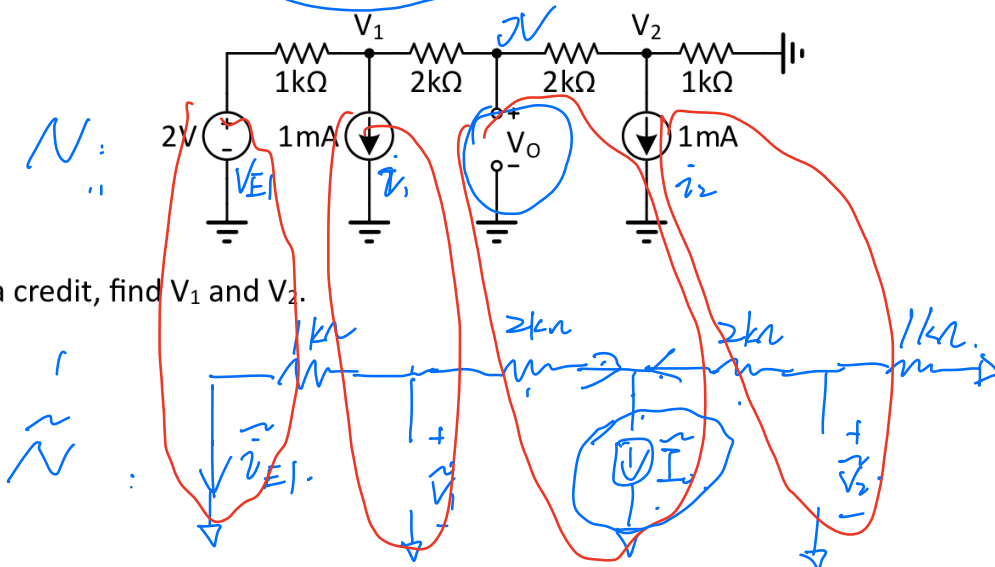2. Analyze the circuit shown using inter-reciprocity.



For extra credit, find  $V_1$  and  $V_2$ .


$$\Rightarrow V_0 \cdot \tilde{I}_0 + V_{EI} \cdot \tilde{I}_{EI} = \tilde{I}_1 \cdot V_1 + \tilde{I}_2 \cdot V_2$$

$$\begin{cases} \tilde{I}_{EI} = -\frac{1}{2} \tilde{I}_0 \\ \tilde{V}_1 = -\frac{1}{2} \tilde{I}_0 R_1 \\ \tilde{V}_2 = -\frac{1}{2} \tilde{I}_0 R_1 \end{cases} \quad \begin{aligned} V_0 &= -V_{EI} \frac{\tilde{I}_{EI}}{\tilde{I}_0} + \tilde{I}_1 \frac{\tilde{V}_1}{\tilde{I}_0} + \tilde{I}_2 \frac{\tilde{V}_2}{\tilde{I}_0} \\ &= 0V \end{aligned}$$

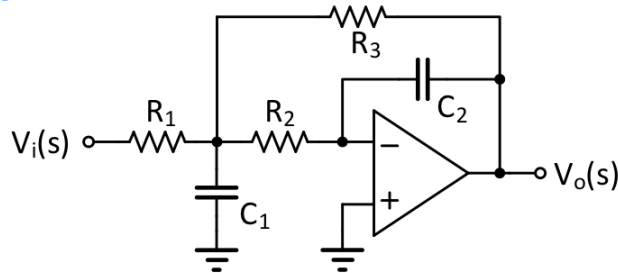3. The Rauch filter shown has a transfer function (assume ideal opamp)

$$H(s) = \frac{1}{s^2 \cdot R_1 \cdot R_2 \cdot C_1 \cdot C_2 + s \cdot C_2 \cdot \left( R_1 + R_2 + \frac{R_1 \cdot R_2}{R_3} \right) + \frac{R_1}{R_3}}$$

If  $R_1 = 2R_2 = 2R_3$  and pole  $Q$  is  $Q = 1/\sqrt{3}$ , what should be the ratio  $C_1/C_2$ ?



For extra credit, find the requirements for the DC gain  $A_0$  and the pole  $Q$  so that the minimum capacitance spread ( $C_1/C_2$  or  $C_2/C_1$ ) can be 1. **Hint:** consider the requirements for  $A_0$  and  $Q$  so that there is real solution for  $R_2/R_3$  when  $C_1 = C_2$ .

$$\begin{aligned}
 H(s) &= \frac{1}{s^2 + \frac{\omega_0}{Q}s + \omega_0^2} \quad \leftarrow \div \frac{1}{R_1 R_2 C_1 C_2} \\
 &= \frac{1}{s^2 + \frac{R_1 + R_2 + \frac{R_1 R_2}{R_3}}{R_1 R_2 C_1} s + \frac{1}{R_2 R_3 C_1 C_2}} \\
 \left\{ \begin{aligned} \frac{R_1 + R_2 + \frac{R_1 R_2}{R_3}}{R_1 R_2 C_1} &= \frac{\omega_0}{Q} & (1) \\ \frac{1}{R_2 R_3 C_1 C_2} &= \omega_0^2 & (2) \end{aligned} \right. \\
 R_1 = 2R_2 = 2R_3, \quad Q = \frac{1}{\sqrt{3}} & \quad (3)
 \end{aligned}$$

$$\omega_0 = \frac{1}{\sqrt{R_3^2 C_1 C_2}}$$

$$\frac{\omega_0}{\frac{1}{\sqrt{3}}} = \frac{\omega_0}{Q} = \frac{R_1 R_3 + R_2 R_3 + R_1 R_2}{R_1 R_2 R_3 C_1}$$

$$= \frac{5}{2 R_2 C_1} = \frac{\sqrt{3}}{R_2 \sqrt{C_1 C_2}}$$

$$\frac{25}{4 C_1^2} = \frac{3}{2 C_2}$$

$$\frac{C_1}{C_2} = \frac{25}{12}$$

$$H(s) = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + \frac{R_1 + R_2 + \frac{R_1 R_2}{R_3}}{R_1 R_2 C_1} s + \frac{1}{R_2 R_3 C_1 C_2}}$$

$\Rightarrow$

$$\text{DC gain} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{\frac{1}{R_2 R_3 C_1 C_2}}$$

$$= \frac{R_3}{R_1}$$

$$\left\{ \begin{array}{l} \frac{R_1 + R_2 + \frac{R_1 R_2}{R_3}}{R_1 R_2 C_1} = \frac{\omega_0}{Q} \\ \frac{1}{R_2 R_3 C_1 C_2} = \omega_0^2 \\ A_0 = \frac{R_3}{R_1} \leftarrow \end{array} \right.$$

$$(1 + A_0)^2 \frac{R_2}{R_3} + \frac{R_3}{R_2} + 2(1 + A_0) = \frac{1}{Q^2} \frac{C_1}{C_2} \leftarrow$$

if  $\frac{C_1}{C_2} = 1$  possible,  $\frac{R_2}{R_3} = X$

$$f(x) = \frac{(1 + A_0)^2 x + \frac{1}{x} + 2(1 + A_0)}{x} \quad \downarrow$$

$$x = \frac{1}{1 + A_0} \quad f(x) \geq 4(1 + A_0)$$

$$\frac{1}{Q^2} \geq (1 + A_0) 4$$

$$Q \leq \frac{1}{2\sqrt{1 + A_0}}$$

