


MIDTERM EXAMINATION

October 25, 2023

Open Book

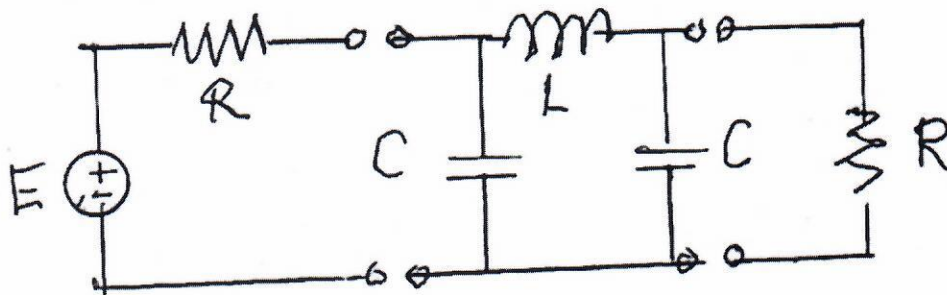
1. Find the **chain matrix** of the two-port shown below.

Extra Credit: Find the **voltage gain** V_2/E if the two-port operates between two equal resistors R . P. 69




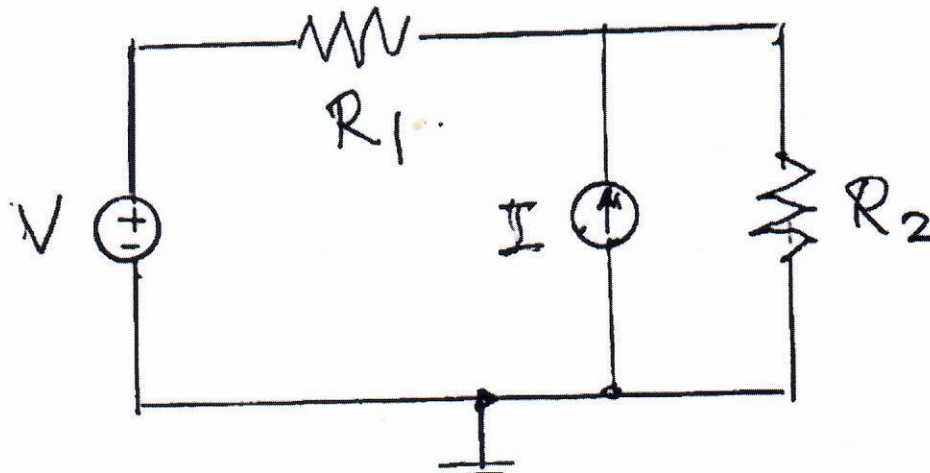2. Construct the **MNA matrix** equations for the circuit shown below.

Extra Credit: Find all **voltages and currents in the circuit**. The element values are $R_1 = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$, $V = 3 \text{ V}$ and $I = 1 \text{ mA}$.




Chain Matrix

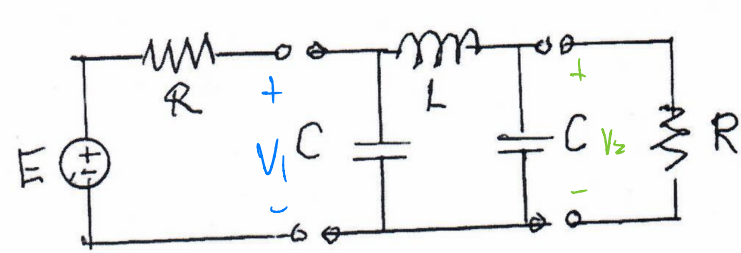

AB - CD

$$\begin{bmatrix} V_1(s) \\ I_1(s) \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2(s) \\ -I_2(s) \end{bmatrix} \Rightarrow \begin{aligned} V_1 &= AV_2 - BI_2 \\ V_2 &= CV_2 - DI_2 \end{aligned}$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0}^{\text{open}} = \frac{sL + \frac{1}{sC}}{\frac{1}{sC}} = s^2LC + 1$$

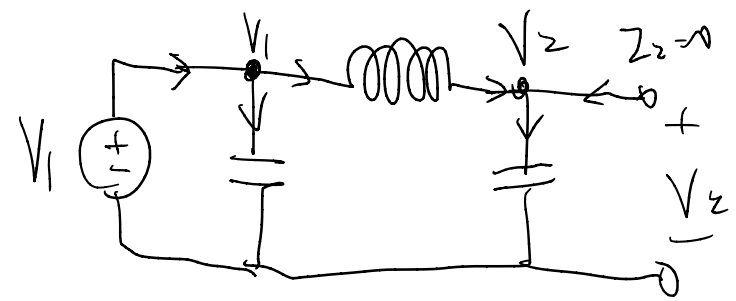


$$\frac{V_1 - V_2}{sL} = sC V_2$$

$$V_1 - V_2 = s^2CL \cdot V_2$$


$$V_1 = V_2 (s^2CL + 1)$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}^{\text{short}} = sL$$

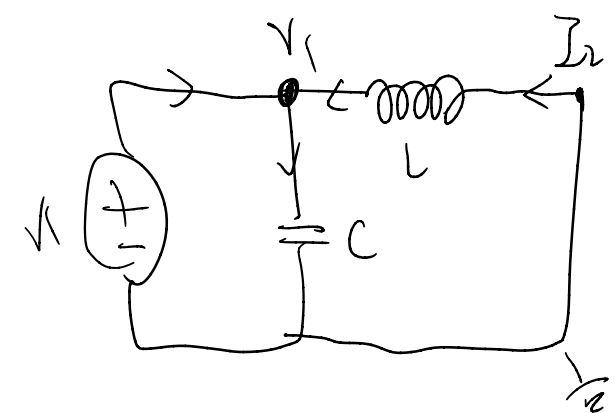


$$I_2 = \frac{0 - V_1}{sL}$$

$$\Rightarrow sL = \frac{V_1}{-I_2}$$

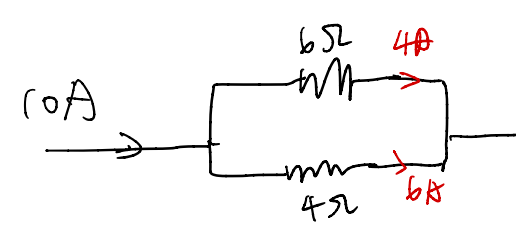


$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0}^{\text{open}}$$

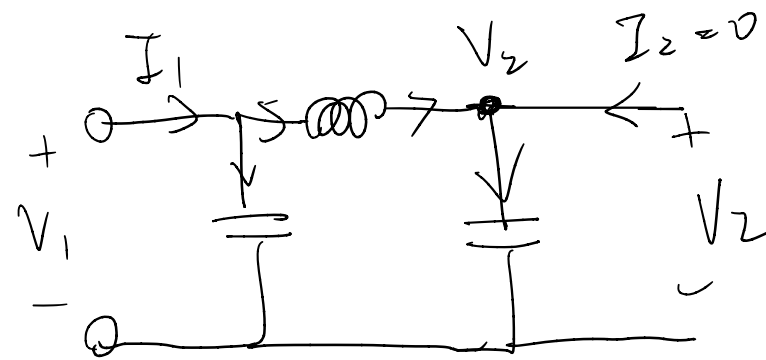

$$1 + s^2LC$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}^{\text{short}}$$

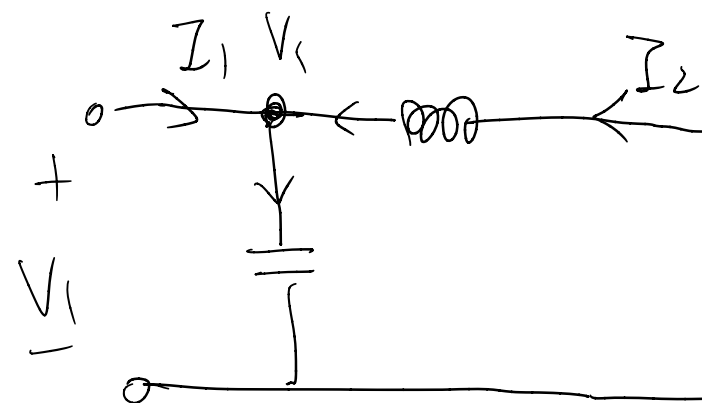

$$sC (s^2LC + 2)$$

$$I_1 = \frac{\frac{1}{sC}}{sL + \frac{1}{sC} + \frac{1}{sC}} \times \frac{1}{sC} = V_2$$

$$I_1 \frac{\left(\frac{1}{sC}\right)^2}{\frac{s^2CL + 2}{sC}} = V_2 \rightarrow \frac{I_1}{V_2} = sC (s^2CL + 2)$$

$$\begin{cases} I_2 = (0 - V_1) \cdot \frac{1}{sL} \rightarrow V_1 = -sL \cdot I_2 \\ I_1 + I_2 = sC V_1 = -s^2CL \cdot I_2 \end{cases}$$

$$\rightarrow I_1 = (-1 - s^2CL) I_2$$

$$\rightarrow \frac{I_1}{-I_2} = 1 + s^2CL$$


(B)

$$A_v = \frac{V_z}{E} = \frac{R_L}{AR_L + B + CR_{GR} + DR_G} = \frac{1}{A + \frac{B}{R} + CR + D}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} s^2LC + 1 & sL \\ sc(s^2CL + 2) & s^2CL + 1 \end{bmatrix}$$

$$= \frac{R}{(s^2LC + 1)R + sL + sc(s^2CL + 2) \cdot R^2 + s^2CLR + R}$$
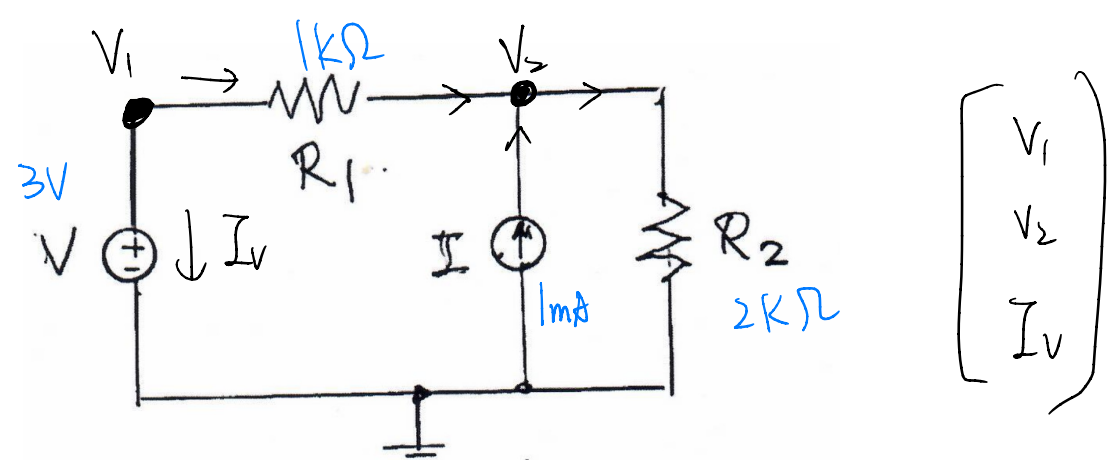
$$= \frac{R}{s^2LCR + R + sL + s^3C^2L R^2 + 2sCR^2 + s^2CLR + R}$$



$$V_1 = 3V$$

$$3 \times 10^{-3} - 5 \times 10^{-4} V_2 + I_V = 0$$

$$(10^{-3} + 5 \times 10^{-4}) V_2 = 10^{-3} + 3 \times 10^{-3}$$

$$10 \times 10^{-4}$$

$$V_2 = \frac{4 \times 10^{-3}}{15 \times 10^{-4}} = \frac{40}{15} = \underline{\underline{\frac{8}{3} V}} \sim 2.67V$$

$$\frac{90}{3}$$

$$30 \times 10^{-4} - \frac{40}{3} \times 10^{-4} + I_V = 0$$

$$I_V = \frac{-5}{3} \times 10^{-3}$$

$$= -1.67mA$$

$$\text{For node 1: } \frac{V_1}{R_1} - \frac{V_2}{R_1} + I_V = 0$$

$$\text{For node 2: } \frac{V_1}{R_1} - \frac{V_2}{R_1} + I = \frac{V_2}{R_2} \Rightarrow \frac{-V_1}{R_1} + \frac{V_2}{R_1} + \frac{V_2}{R_2} = I$$

$$\text{For Voltage source: } V_1 = V$$

$$\begin{bmatrix} \frac{1}{R_1} & -\frac{1}{R_1} & 1 \\ -\frac{1}{R_1} & \frac{1}{R_1} + \frac{1}{R_2} & 0 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ I_V \end{bmatrix} = \begin{bmatrix} 0 \\ I \\ V \end{bmatrix}$$