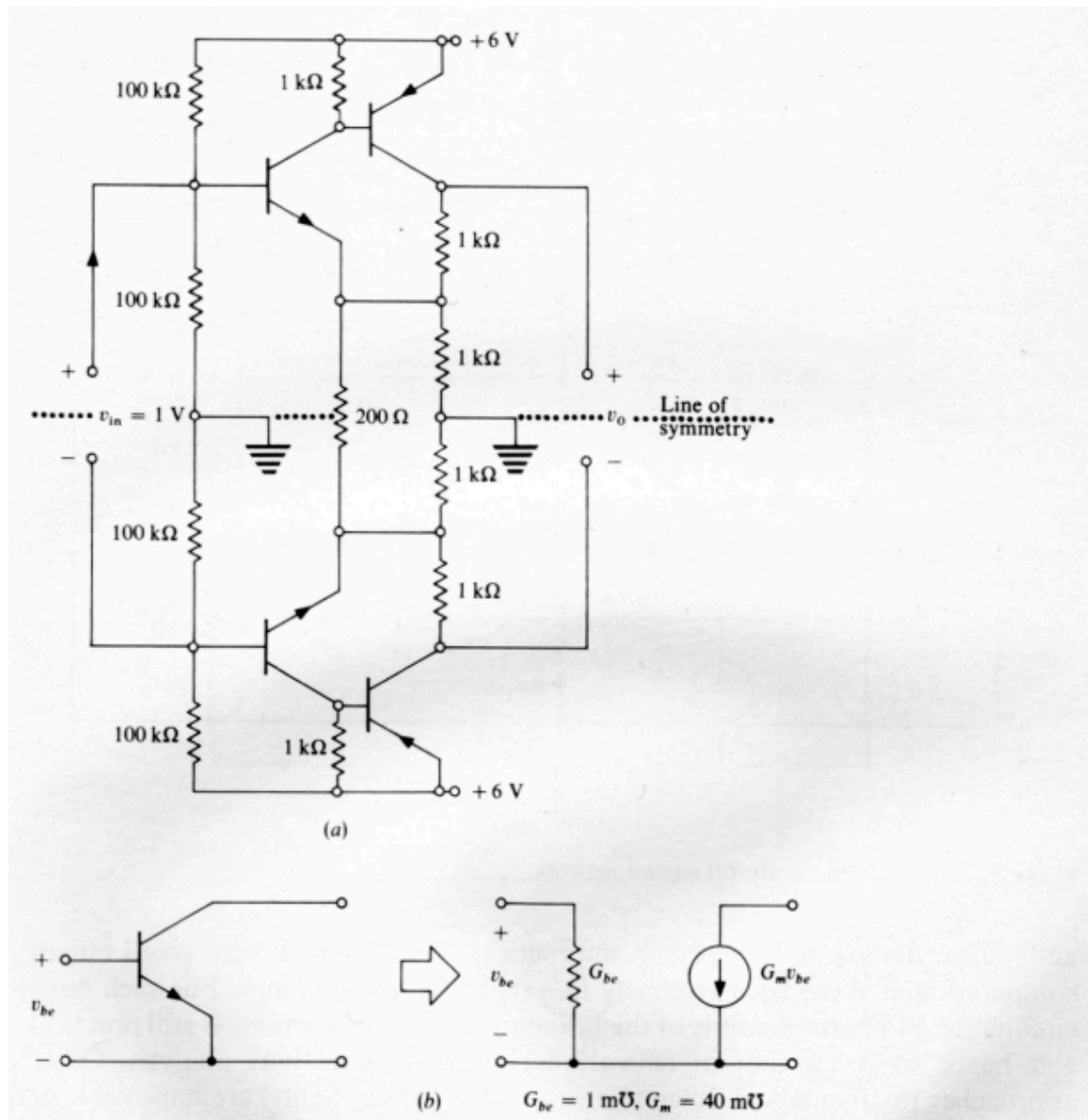


SENSITIVITIES OF A BJT OPAMP



Half circuit, and its adjoint network: